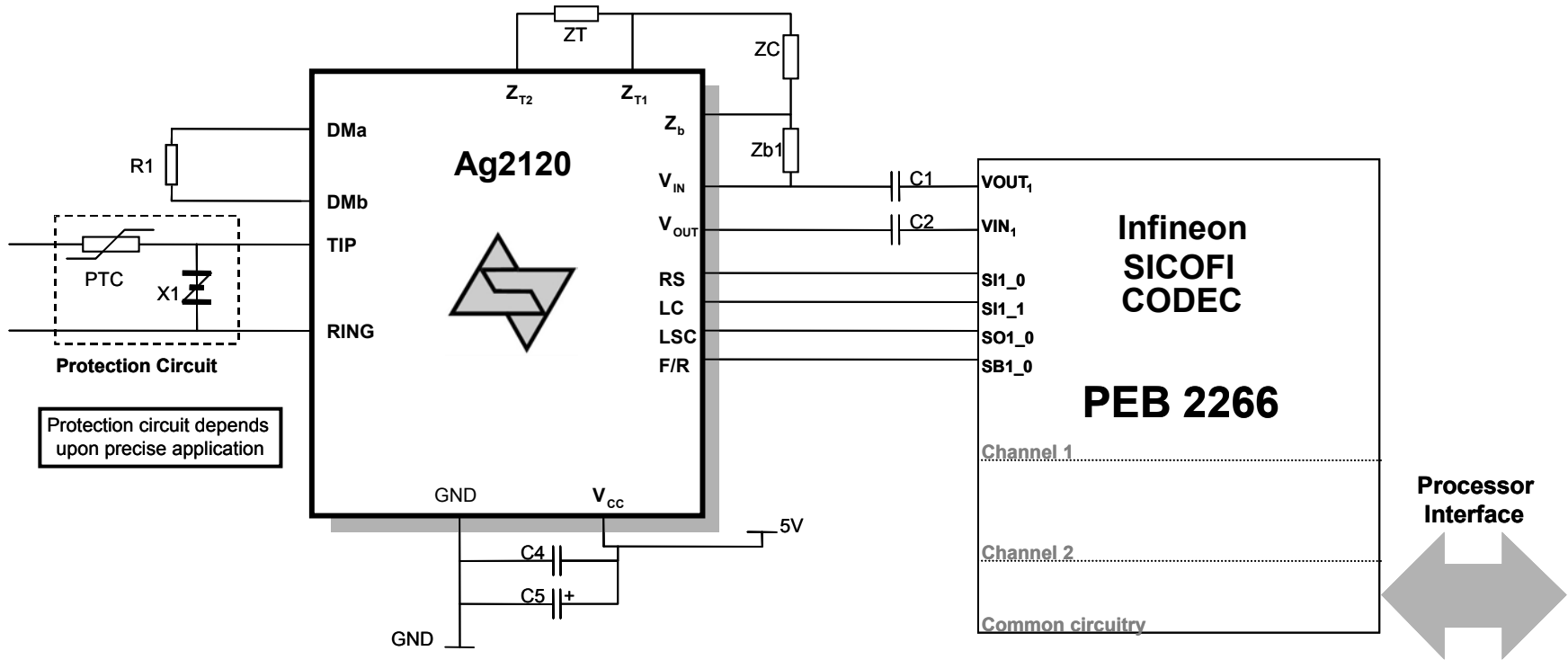


Interfacing Ag2120 to Infineon PEB2266



For 600R line and balance impedance:	R1 = 390k
	Zb1 = 100k
	ZC = 47k
	ZT = 300R
	C1, C2, C4 = 100nF
	C5 = 10uF
Typical protection:	PTC = TR600-150 (Raychem)
	X1 = P2600SA (Teccor)