

TEST CIRCUITS FOR PSTN INTERFACES

Silver Telecom Product Datasheets contain an Applications Diagram. This shows the electrical connections and typical values of external components required, when using our products.


Always consult the datasheet before performing parametric testing.

The basic parametric test circuits, used by Silver Telecom when testing PSTN Interfaces, are shown on the following pages.

Note that the PSTN interface may be known as a COIC, DAA or FXO interface. This depends on the application in which it is used.


TEST CIRCUITS FOR PSTN INTERFACES

DC ELECTRICAL TESTS

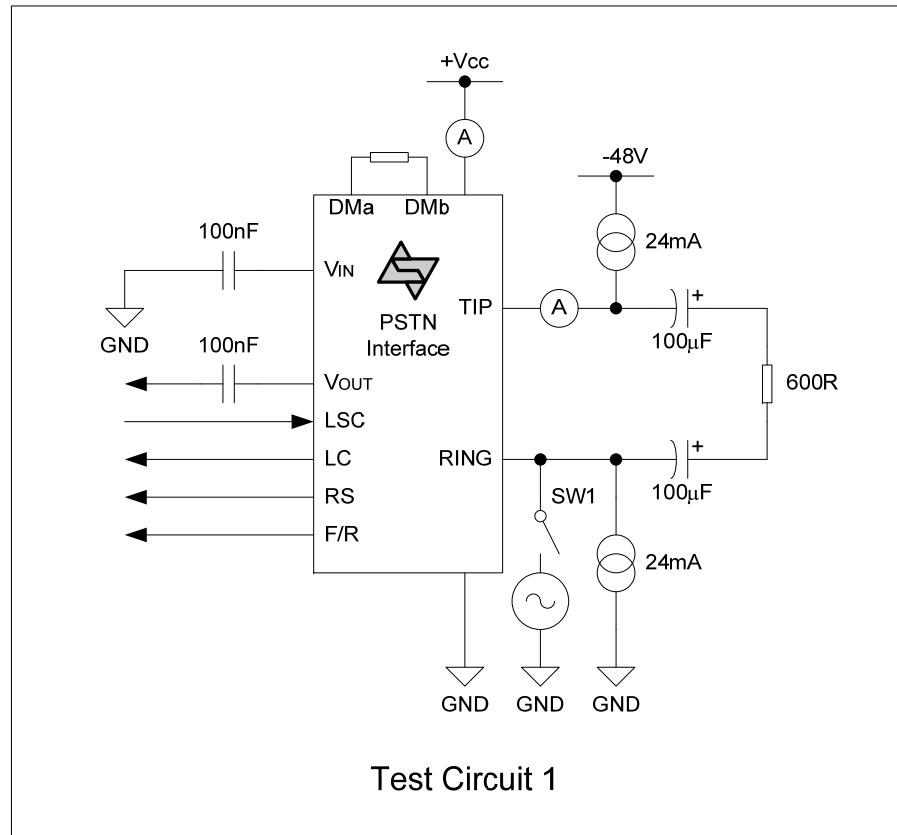

TEST CIRCUITS FOR PSTN INTERFACES


TRANSMIT GAIN TEST (2W TO 4W)

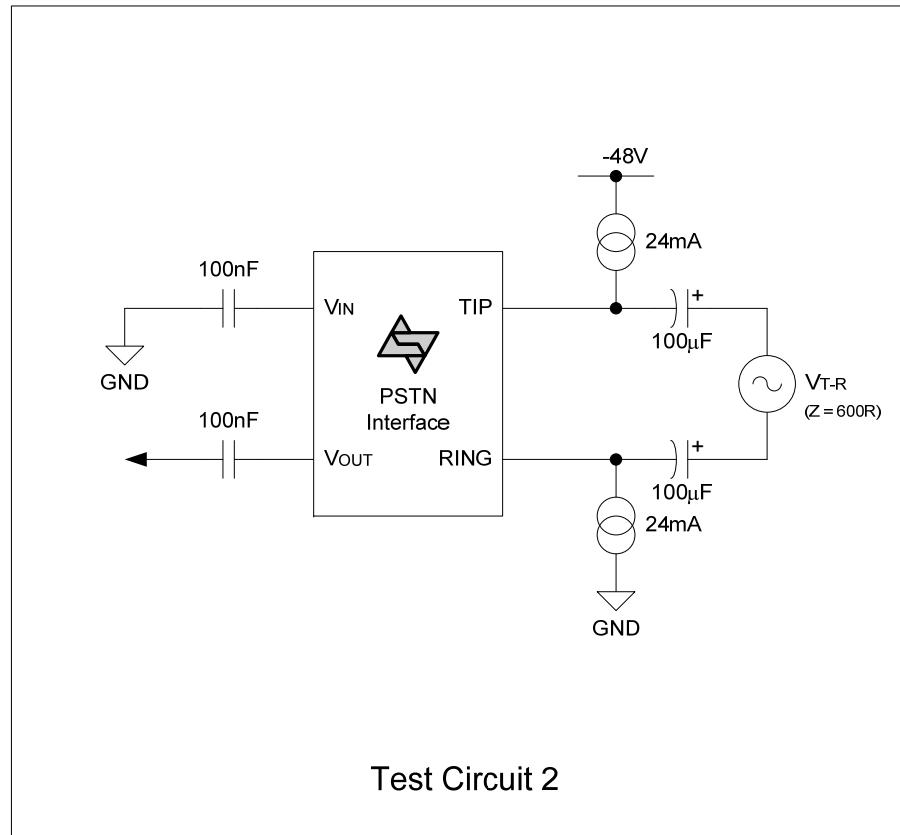

$$\text{Transmit Gain} = 20 \log(V_{\text{OUT}} / V_{\text{T-R}})$$

TEST CIRCUITS FOR PSTN INTERFACES

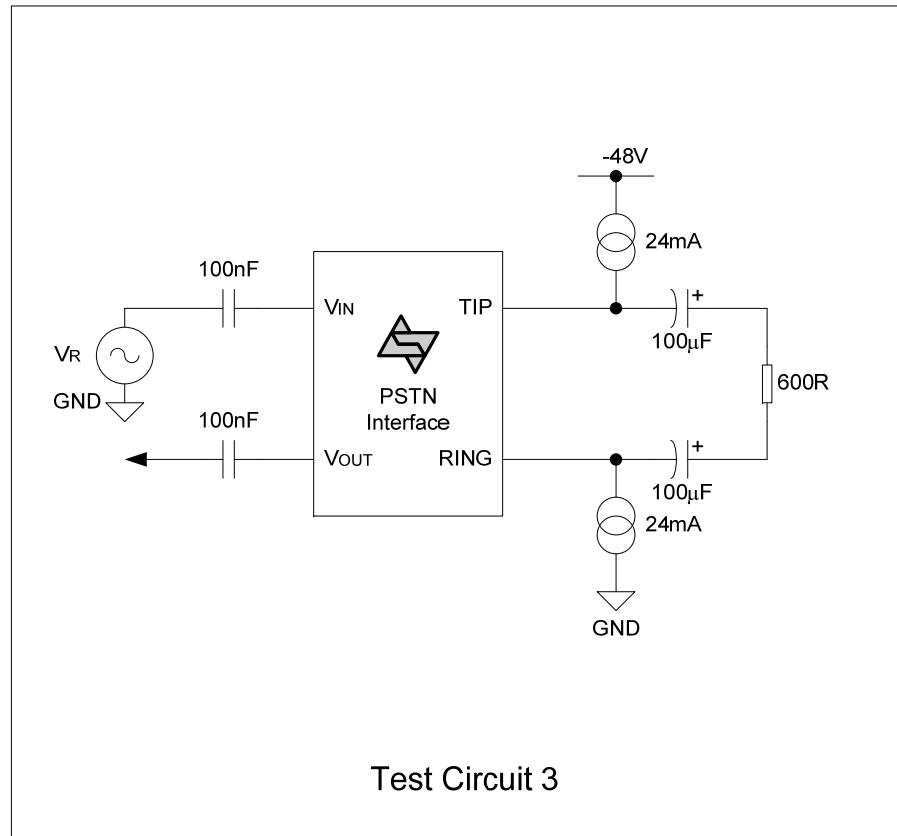RECEIVE GAIN TEST (4W TO 2W) AND TRANS HYBRID LOSS




$$\text{Receive Gain} = 20 \log(V_{T-R} / V_{IN})$$

$$\text{Trans Hybrid Loss} = 20 \log(V_{OUT} / V_{IN})$$

TEST CIRCUITS FOR PSTN INTERFACES

CMESSAGE NOISE AT 4W AND 2W

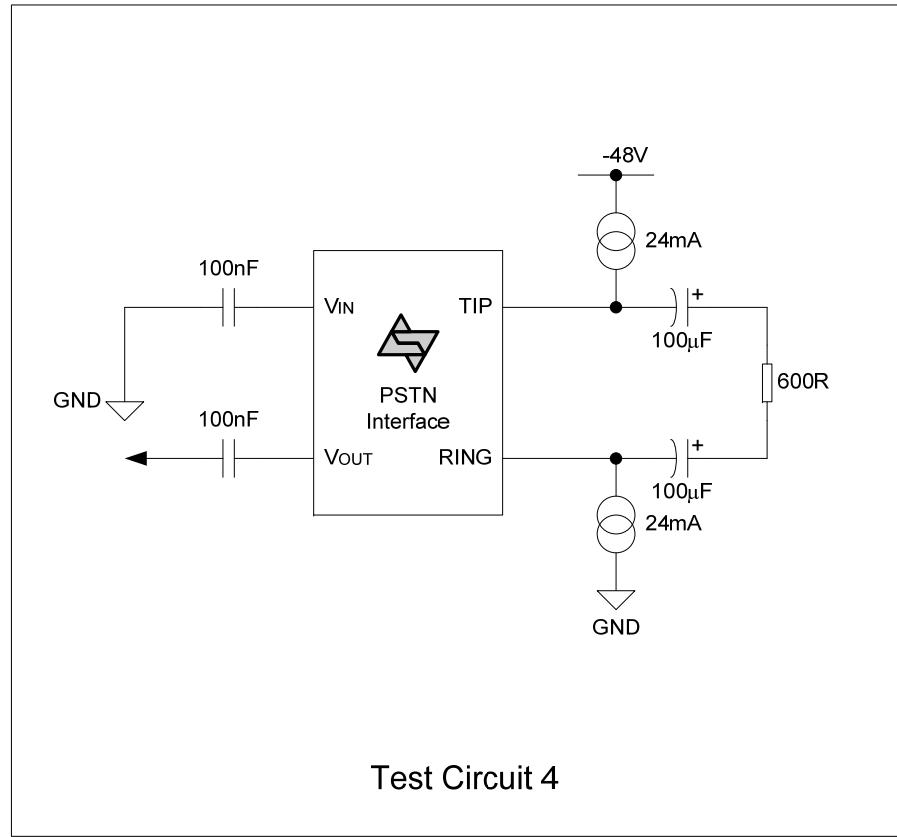


$4W \text{ Noise} = 20 \log(V_{T-R} / 0.775)$ NOTE: V_{T-R} with a Cmess Filter

$2W \text{ Noise} = 20 \log(V_{OUT} / 0.775)$ NOTE: V_{OUT} with a Cmess Filter

TEST CIRCUITS FOR PSTN INTERFACES


RETURN LOSS

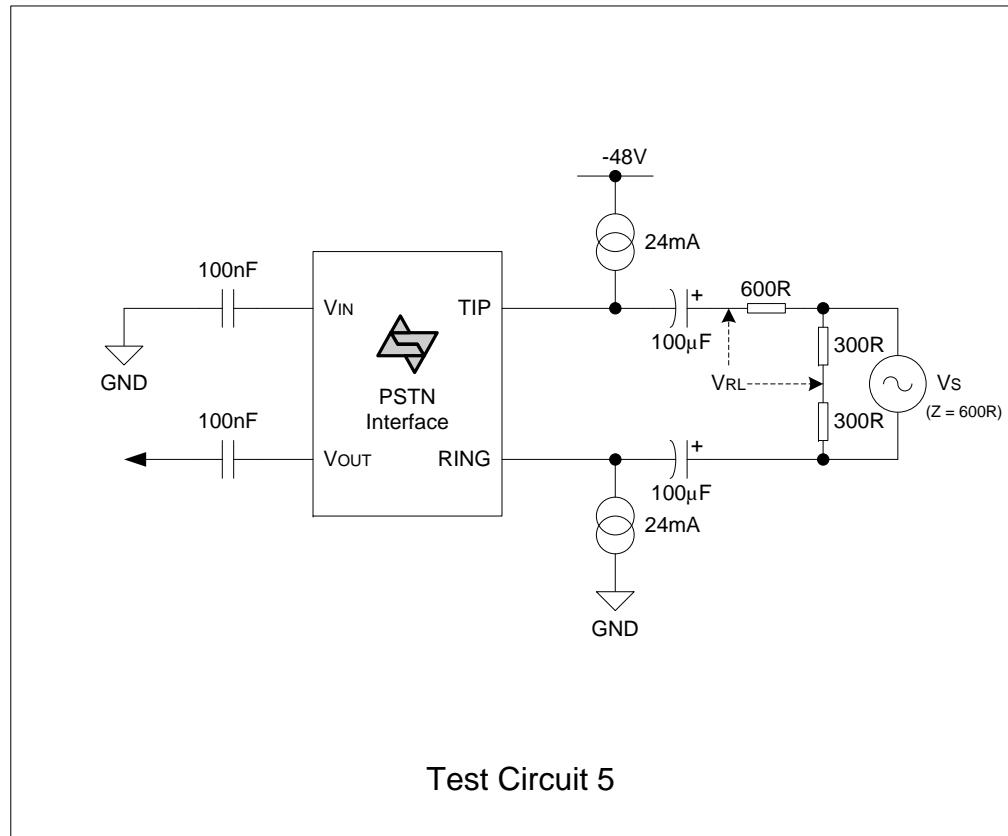

$$\text{Return Loss} = 20 \log(2V_{RL} / V_S)$$

TEST CIRCUITS FOR PSTN INTERFACES

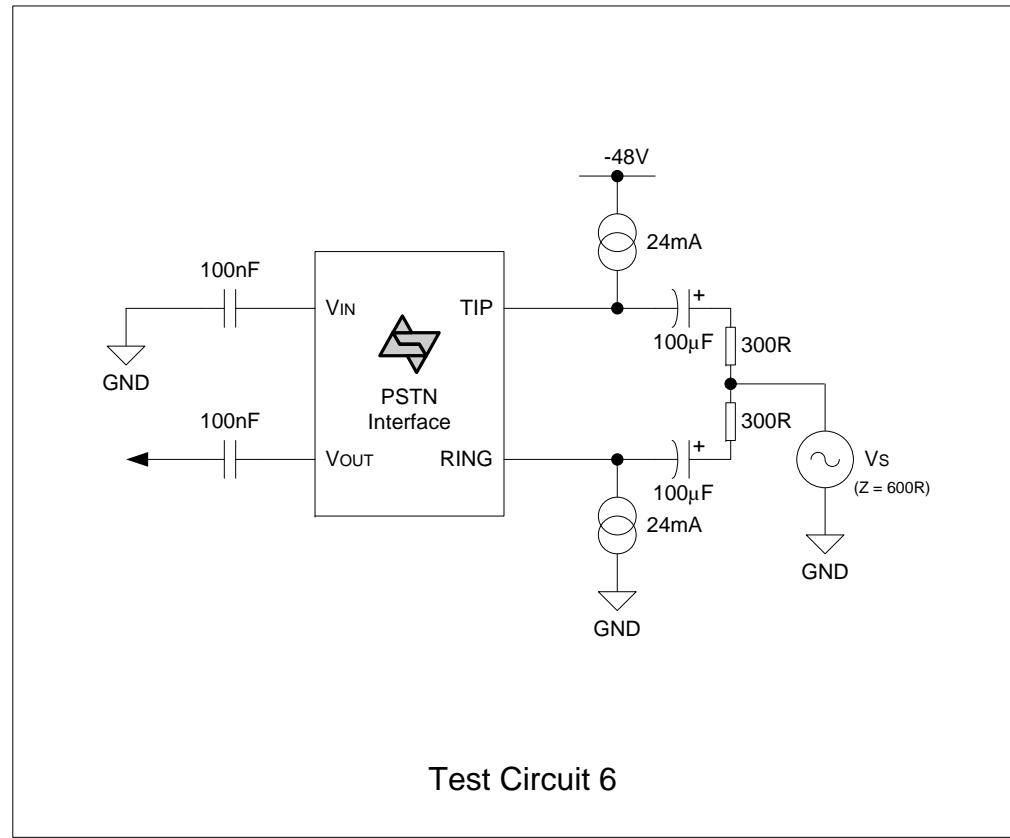CMRR AND LONGITUDINAL TO METALLIC BALANCE




$$CMRR = 20 \log(V_{OUT} / V_S)$$

$$\text{Longitudinal To Metallic Balance} = 20 \log(V_{T-R} / V_S)$$

TEST CIRCUITS FOR PSTN INTERFACES

METALLIC TO LONGITUDINAL BALANCE

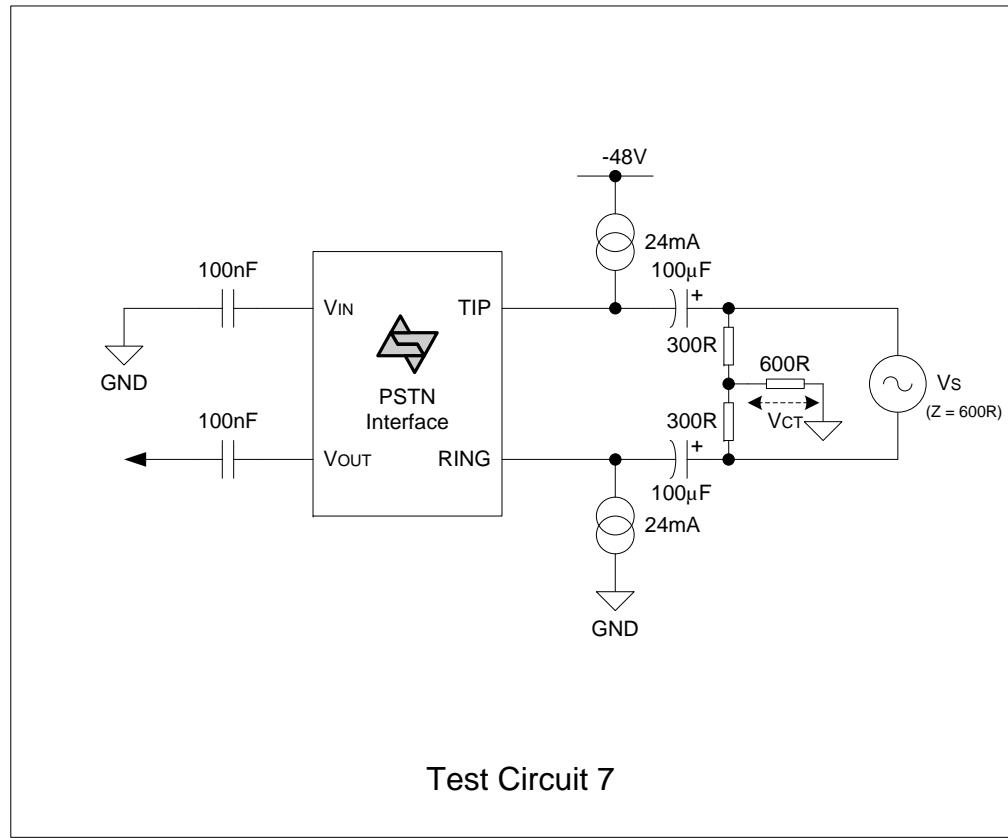

$$\text{Metallic to Longitudinal Balance} = 20 \log(2V_{CT} / V_{T-R})$$